
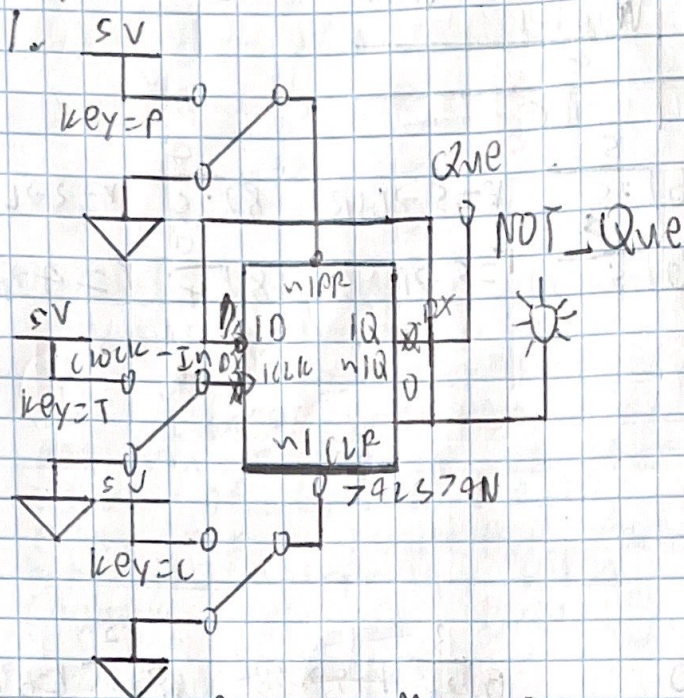


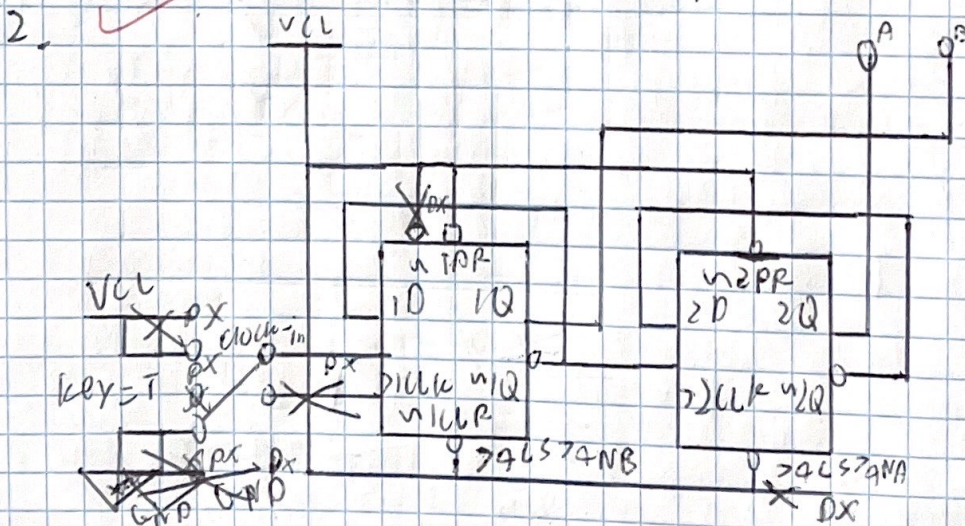Activity 1.2.4 Introduction to Sequential Logic Design



- ~~On Multisim~~
- The circuit works like the circuit in 1.10.
- ~~Que~~ is lit up and ~~NOT-Que~~ is not lit.
- The state of the outputs do not change.
- ~~Que~~ is off, while ~~NOT-Que~~ is on.
- The state of the outputs does not change.



Signature *[Signature]*

Signature *[Signature]*

Date 11/10/21

Date 11/10/21

continued on page 45

Proprietary Information

d. On Multisim

clock-in	A	B
Initial values	0	0
cycle 1	0	1
cycle 2	1	0
cycle 3	1	1
cycle 4	0	0
cycle 5	0	1
cycle 6	1	0
cycle 7	1	1
cycle 8	0	0
cycle 9	0	1

c. The cycle starts with A and B both as 0. The sequence of combinations A=0 and B=0, A=0 and B=1, A=1 and B=0, and A=1 and B=1 repeats every fourth cycle.

The 01P create a binary count from 0 to 30 (00₂ to 11₂)

3. a-d. On Multisim

Signal	Period	Frequency
clock-in	20ms / div = 10ms	$f = \frac{1}{T} = \frac{1}{10 \times 10^{-3} \text{ s}} = 10^3 = 1000 \text{ Hz}$
B	20ms / div = 12ms	$f = \frac{1}{T} = \frac{1}{12 \times 10^{-3} \text{ s}} = 83.33 \text{ Hz}$
A	3.2 div. 20ms = 64ms	$f = \frac{1}{T} = \frac{1}{64 \times 10^{-3} \text{ s}} = 15.625 \text{ Hz}$

f. The periods and frequency are inversely proportional to each other. The frequency of the clock-in is two times that of the signal B.

Signature [Signature]

Date 11/17/21


Continued on page 46

Signature

Date

Proprietary In format 10%

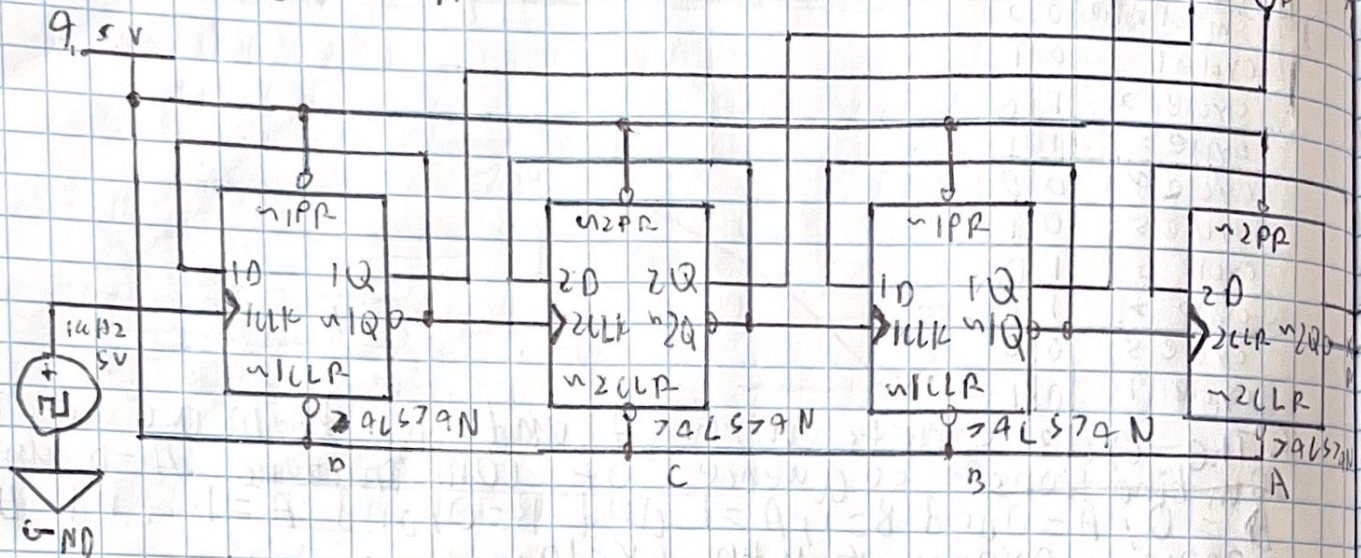and the frequency of signal B is double of signal A.



Signal	Period	frequency
Clock-in	$T = \frac{1}{f}$ $= \frac{1}{1000\text{Hz}}$ $T = 0.001\text{s}$	1000Hz
D	$0.8 \div 20\text{ms}$ $= 1\text{ms}$	$f = \frac{1}{T}$ $= \frac{1}{1\text{ms}}$ $= \frac{1}{1 \times 10^{-3}\text{s}}$ $= 1000$ $= 1000\text{Hz}$
C	$0.2 \div 20\text{ms}$ $= 0.1\text{ms}$	$f = \frac{1}{T}$ $= \frac{1}{0.1\text{ms}}$ $= \frac{1}{0.1 \times 10^{-3}\text{s}}$ $= \frac{1}{0.0001\text{s}}$ $= 10000$ $= 10000\text{Hz}$
B	$0.4 \div 20\text{ms}$ $= 0.2\text{ms}$	$f = \frac{1}{T}$ $= \frac{1}{0.2\text{ms}}$ $= \frac{1}{0.2 \times 10^{-3}\text{s}}$ $= \frac{1}{0.0002\text{s}}$ $= 5000$ $= 5000\text{Hz}$

Signature *[Signature]*

Signature *[Signature]*

Date 11/18/21

Continued on page 42

Date 11/19/21

Proprietary Information

A $0.8 \mu\text{V} \cdot \frac{20 \text{ ms}}{1 \mu\text{V}}$

$= 16 \text{ ms}$

$f = \frac{1}{16 \text{ ms}}$

$= \frac{1}{16 \cdot 10^{-3} \text{ s}}$

$= 103$

$= \frac{16 \text{ s}}{62.5 \text{ Hz}}$

9. a. 1, 10, 11, 100, 101, 110, 111, 1000, 1001, 1010, 1011, 1100, 1101, 1110, 1111
b. A clock frequency of 1 Hz works best for me.

Conclusion

- Conclusion -
1. Each counter^{probe} to the left of another blinks twice as fast as the counter on its right. If a probe that is on is represented by a 1 and a probe that is off is represented by a 0, the counter loops through the numbers 0-15. The relative blink speeds of the probes contribute to how they produce the effect of counting in binary repeatedly.
 2. The highest number I can count to is 31.
 3. One product is a digital clock, which uses a counter to measure time. Another product is a fire alarm, which uses a counter to make sure the time between each time it makes a noise is constant. Another ~~object~~^{product} is a car, as it^{in which} uses a counter to make the frequency constant when it flashes its lights.